
Driven Series RLC Circuit

Laplace solution of non-homogeneous 2nd order differential equation

John Morrow

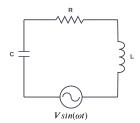

Series RLC Circuit with sinusoidal driving function

The Kirchhoff voltage equation for the series RLC circuit with a driving function, f(t), is given by:

$$L\frac{di}{dt} + Ri + \frac{1}{C} \int i \, dt = f(t) \tag{1}$$

Take the derivative of Equation 1 to remove the integral:

$$\frac{di^2}{dt^2} + \lambda \frac{di}{dt} + \omega_0^2 i = \frac{1}{L} f'(t) \tag{2}$$

where,

$$\lambda = \frac{R}{L} \qquad \omega_0 = \frac{1}{\sqrt{LC}} \tag{3}$$

For a sinusoidal driving function:

$$f(t) = V sin(\omega t) \tag{4}$$

Applying the driving function, Equation 2 becomes:

$$\frac{di^2}{dt^2} + \lambda \frac{di}{dt} + \omega_0^2 i = \frac{V\omega}{L} cos(t)$$
 (5)

The solution to Equation 5 comprises a steady state response and a transient response.

$$i(t) = i(t)_{transient} + i(t)_{steady\ state}$$
(6)

The transient response has three possibilities depending on whether the circuit is under-damped, overdamped, or critically-damped. The steady-state and transient responses are derived below.

Derivation of the solution

The initial conditions required to solve the differential equation are given by:

$$i(t)\Big|_{t=0} = 0 \tag{7}$$

$$i(t)' = \frac{di}{dt}\Big|_{t=0} = 0 \tag{8}$$

The initial condition in Equation 8 is derived from the Kirchhoff voltage equation. At t=0, the capacitor, C, has an initial charge of Q=0, yielding a capacitor voltage of $V_C=\frac{Q}{C}=0$. Also, since i(0)=0 (Equation 7), the voltage across the resistor, R, is $V_R=iR=0$. The driving voltage at t=0 is $f(t)=Vsin(\omega t)=0$. Therefore, the voltage equation around the circuit reduces to $V_L=L\frac{di}{dt}=0$, where V_L is the voltage across the inductor, L. Since L>0, $\frac{di}{dt}=0$.

Take the Laplace transform of Equation 5:

$$s^{2}I(s) - si(o) - si'(0) + \lambda sI(s) - \lambda si(0) + \omega_{0}^{2}I(s) = \frac{V\omega}{L} \frac{s}{s^{2} + \omega^{2}}$$
(9)

Apply the initial conditions:

$$s^2I(s) + \lambda sI(s) + \omega_0^2I(s) = \frac{V\omega}{L}\frac{s}{s^2 + \omega^2} \tag{10} \label{eq:10}$$

Solve for I(s):

$$I(s) = \frac{V\omega}{L} \frac{s}{(s^2 + \omega^2)(s^2 + \lambda s + \omega_0^2)}$$

$$\tag{11}$$

Apply partial fraction decomposition:

$$I(s) = \frac{V\omega}{L} \left(\frac{As+B}{s^2 + \omega^2} + \frac{Cs+D}{s^2 + \lambda s + \omega_0^2} \right) \tag{12}$$

$$= \frac{V\omega}{L} \left(\frac{(As+B)(s^2 + \lambda s + \omega_0^2) + (Cs+D)(s^2 + \omega^2)}{(s^2 + \omega^2)(s^2 + \lambda s + \omega_0^2)} \right)$$
(13)

Set the numerators of Equation 11 and Equation 13 equal, expand, and collect on similar powers of s:

$$s = (A + C)s^{3} + (A\lambda + B + D)s^{2} + (A\omega_{0}^{2} + B\lambda + C\omega^{2})s + B\omega_{0}^{2} + D\omega^{2}$$
(14)

Set the coefficients of similar powers of s equal:

$$s^3: 0 = A + C (15)$$

$$s^2: 0 = A\lambda + B + D (16)$$

$$s^1: 1 = A\omega_0^2 + B\lambda + C\omega^2$$
 (17)

$$s^0: 0 = B\omega_0^2 + D\omega^2 (18)$$

Determine A, B, C, and D from the simultaneous equations, s^3 , s^2 , s^1 , and s^0 :

$$A = \frac{-\omega^2 + \omega_0^2}{Den} \quad B = \frac{\lambda \omega^2}{Den} \quad C = \frac{\omega^2 - \omega_0^2}{Den} \quad D = \frac{-\lambda \omega_0^2}{Den}$$
 (19)

where,

$$Den = (\omega^2 - \omega_0^2)^2 + \lambda^2 \omega^2 \tag{20}$$

Apply A, B, C, and D to Equation 12:

$$I(s) = \frac{V\omega}{L \cdot Den} \left(\frac{s(-\omega^2 + \omega_0^2) + \lambda\omega^2}{s^2 + \omega^2} + \frac{s(\omega^2 - \omega_0^2) - \lambda\omega_0^2}{s^2 + \lambda s + \omega_0^2} \right) \tag{21}$$

Steady-state response

The steady-state response is derived from the left-hand term of Equation 21:

$$I(s)_{steady_state} = \frac{V\omega}{L \cdot Den} \left(\frac{s(-\omega^2 + \omega_0^2) + \lambda \omega^2}{s^2 + \omega^2} \right)$$
 (22)

$$= \frac{V\omega}{L \cdot Den} \left(\frac{-s\omega^2}{s^2 + \omega^2} + \frac{s\omega_0^2}{s^2 + \omega^2} + \frac{\lambda\omega^2}{s^2 + \omega^2} \right)$$
 (23)

Take the inverse Laplace transform of Equation 23:

$$i(t)_{steady_state} = \frac{V\omega}{L \cdot Den} \left(-\omega^2 cos(\omega t) + \omega_0^2 cos(\omega t) + \lambda \omega sin(\omega t) \right)$$
 (24)

$$=\frac{V\omega}{L\cdot Den}\Big((\omega_0^2-\omega^2)cos(\omega t)+\lambda\omega sin(\omega t)\Big) \tag{25}$$

Transient response

The transient response is derived from the right-hand term of Equation 21:

$$I(s)_{transient} = \frac{V\omega}{L \cdot Den} \left(\frac{s(\omega^2 - \omega_0^2) - \lambda \omega_0^2}{s^2 + \lambda s + \omega_0^2} \right)$$
 (26)

$$= \frac{V\omega}{L \cdot Den} \left(\frac{s(\omega^2 - \omega_0^2) - \lambda \omega_0^2}{(s + \frac{\lambda}{2} + \mu)(s + \frac{\lambda}{2} - \mu)} \right) \tag{27}$$

where,

$$\mu = \sqrt{\left| \left(\frac{\lambda}{2} \right)^2 - \omega_0^2 \right|} \tag{28}$$

under-damped case

For the under-damped case, where $\left(\frac{\lambda}{2}\right)^2-\omega_0^2<0$, Equation 27 becomes:

(note:
$$j = \sqrt{-1}$$
)

$$I(s)_{transient} = \frac{V\omega}{L \cdot Den} \left(\frac{s(\omega^2 - \omega_0^2) - \lambda \omega_0^2}{(s + \frac{\lambda}{2} + j\mu)(s + \frac{\lambda}{2} - j\mu)} \right)$$
(29)

Apply partial fraction decomposition:

$$I(s)_{transient} = \frac{V\omega}{L \cdot Den} \left(\frac{G}{s + \frac{\lambda}{2} + j\mu} + \frac{H}{s + \frac{\lambda}{2} - j\mu} \right) \tag{30}$$

$$=\frac{V\omega}{L\cdot Den}\left(\frac{G(s+\frac{\lambda}{2}-j\mu)+H(s+\frac{\lambda}{2}+j\mu)}{(s+\frac{\lambda}{2}+j\mu)(s+\frac{\lambda}{2}-j\mu)}\right) \tag{31}$$

Set the numerators of Equation 29 and Equation 31 equal, expand, and collect on similar powers of s:

$$s(\omega^2 - \omega_0^2) - \lambda \omega_0^2 = G(s + \frac{\lambda}{2} - j\mu) + H(s + \frac{\lambda}{2} + j\mu)$$
 (32)

$$s(\omega^2 - \omega_0^2) - \lambda \omega_0^2 = s(G+H) + G(\frac{\lambda}{2} - j\mu) + H(\frac{\lambda}{2} + j\mu)$$
 (33)

Set the coefficients of similar powers of s equal:

$$s^1: \quad \omega^2 - \omega_0^2 = G + H$$
 (34)

$$s^{0}: \quad -\lambda\omega_{0}^{2} = G(\frac{\lambda}{2} - j\mu) + H(\frac{\lambda}{2} + j\mu)$$
 (35)

Determine G and H from simultaneous equations s^1 and s^0 :

$$G = -jP + Q (36)$$

$$H = jP + Q \tag{37}$$

where,

$$P = \frac{\lambda}{4\mu}(\omega^2 + \omega_0^2) \tag{38}$$

$$Q = \frac{1}{2}(\omega^2 - \omega_0^2)$$
 (39)

Apply G and H to Equation 30:

$$I(s)_{transient} = \frac{V\omega}{L \cdot Den} \left(\frac{-jP + Q}{s + \frac{\lambda}{2} + j\mu} + \frac{jP + Q}{s + \frac{\lambda}{2} - j\mu} \right) \tag{40}$$

Take the inverse Laplace transform of Equation 40:

$$i(t)_{transient} = \frac{V\omega}{L \cdot Den} \left(-jP \, e^{-(\frac{\lambda}{2} + j\mu)t} + Q \, e^{-(\frac{\lambda}{2} + j\mu)t} + jP \, e^{-(\frac{\lambda}{2} - j\mu)t} + Q \, e^{-(\frac{\lambda}{2} - j\mu)t} \right) \tag{41}$$

$$=\frac{V\omega}{L\cdot Den}\,e^{-\frac{\lambda}{2}t}\left(jP\Big(-e^{-j\mu t}+e^{j\mu t}\Big)+Q\Big(e^{-j\mu t}+e^{j\mu t}\Big)\right) \tag{42}$$

$$=\frac{V\omega}{L\cdot Den}\,e^{-\frac{\lambda}{2}t}\left(-2P\Big(\frac{-e^{-j\mu t}+e^{j\mu t}}{2j}\Big)+2Q\Big(\frac{e^{-j\mu t}+e^{j\mu t}}{2}\Big)\right) \tag{43}$$

$$i(t)_{transient} = \frac{V\omega}{L \cdot Den} e^{-\frac{\lambda}{2}t} \left(-2P \sin(\mu t) + 2Q \cos(\mu t) \right)$$
 (44)

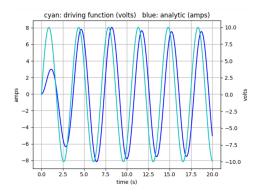


Figure 2: under-damped transient + steady-state $R=1.0,\,L=1.51,\,C=0.3,\,\omega=1.8,\,V=10$

over-damped case

For the over-damped case, where $\left(\frac{\lambda}{2}\right)^2-\omega_0^2>0$, Equation 27 becomes:

$$I(s)_{transient} = \frac{V\omega}{L \cdot Den} \left(\frac{s(\omega^2 - \omega_0^2) - \lambda \omega_0^2}{(s + \frac{\lambda}{2} + \mu)(s + \frac{\lambda}{2} - \mu)} \right)$$
(45)

Apply partial fraction decomposition:

$$I(s)_{transient} = \frac{V\omega}{L \cdot Den} \left(\frac{G}{s + \frac{\lambda}{2} + \mu} + \frac{H}{s + \frac{\lambda}{2} - \mu} \right) \tag{46}$$

$$= \frac{V\omega}{L \cdot Den} \left(\frac{G(s + \frac{\lambda}{2} - \mu) + H(s + \frac{\lambda}{2} + \mu)}{(s + \frac{\lambda}{2} + \mu)(s + \frac{\lambda}{2} - \mu)} \right) \tag{47}$$

Set the numerators of Equation 45 and Equation 47 equal, expand, and collect on similar powers of s:

$$s(\omega^2 - \omega_0^2) - \lambda \omega_0^2 = G(s + \frac{\lambda}{2} - \mu) + H(s + \frac{\lambda}{2} + \mu)$$

$$\tag{48}$$

$$s(\omega^2 - \omega_0^2) - \lambda \omega_0^2 = s(G+H) + G(\frac{\lambda}{2} - \mu) + H(\frac{\lambda}{2} + \mu)$$

$$\tag{49}$$

Set the coefficients of similar powers of s equal:

$$s^1: \qquad \omega^2 - \omega_0^2 = G + H$$
 (50)

$$s^{0}: \quad -\lambda\omega_{0}^{2} = G(\frac{\lambda}{2} - \mu) + H(\frac{\lambda}{2} + \mu)$$
 (51)

Determine G and H from simultaneous equations s^1 and s^0 :

$$G = P + Q (52)$$

$$H = -P + Q (53)$$

where,

$$P = \frac{\lambda}{4\mu}(\omega^2 + \omega_0^2) \tag{54}$$

$$Q = \frac{1}{2}(\omega^2 - \omega_0^2) \tag{55}$$

Apply G and H to Equation 46:

$$I(s)_{transient} = \frac{V\omega}{L \cdot Den} \left(\frac{P+Q}{s+\frac{\lambda}{2}+\mu} + \frac{-P+Q}{s+\frac{\lambda}{2}-\mu} \right) \tag{56}$$

Take the inverse Laplace transform of Equation 56:

$$i(t)_{transient} = \frac{V\omega}{L \cdot Den} e^{-\frac{\lambda}{2}t} \left(P\left(e^{-\mu t} - e^{\mu t}\right) + Q\left(e^{-\mu t} + e^{\mu t}\right) \right)$$
 (57)

$$i(t)_{transient} = \frac{V\omega}{L \cdot Den} e^{-\frac{\lambda}{2}t} \left(\left(P + Q \right) e^{-\mu t} + \left(Q - P \right) e^{\mu t} \right)$$
 (58)

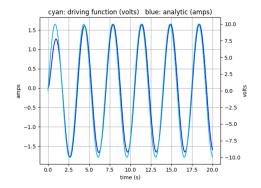


Figure 3: over-damped transient + steady-state

$$R=6.0$$
 , $L=1.51$, $C=0.3$, $\omega=1.8$, $V=10$

critically-damped case

For the critically-damped case, where $\left(\frac{\lambda}{2}\right)^2-\omega_0^2=0$ and $\mu=0$, Equation 27 becomes:

$$I(s)_{transient} = \frac{V\omega}{L \cdot Den} \left(\frac{s(\omega^2 - \omega_0^2) - \lambda \omega_0^2}{(s + \frac{\lambda}{2})(s + \frac{\lambda}{2})} \right)$$
 (59)

Apply partial fraction decomposition:

$$I(s)_{transient} = \frac{V\omega}{L \cdot Den} \left(\frac{G}{(s + \frac{\lambda}{2})} + \frac{H}{(s + \frac{\lambda}{2})^2} \right)$$
 (60)

$$= \frac{V\omega}{L \cdot Den} \left(\frac{G(s + \frac{\lambda}{2}) + H}{(s + \frac{\lambda}{2})^2} \right) \tag{61}$$

Set the numerators of Equation 59 and Equation 61 equal, expand, and collect on similar powers of s:

$$s(\omega^2 - \omega_0^2) - \lambda \omega_0^2 = G(s + \frac{\lambda}{2}) + H \tag{62}$$

$$s(\omega^2 - \omega_0^2) - \lambda \omega_0^2 = sG + G\frac{\lambda}{2} + H \tag{63}$$

Set the coefficients of similar powers of \boldsymbol{s} equal:

$$s^1: \omega^2 - \omega_0^2 = G$$
 (64)

$$s^0: \quad -\lambda\omega_0^2 = G\frac{\lambda}{2} + H \tag{65}$$

Determine G and H from simultaneous equations s^1 and s^0 :

$$G = \omega^2 - \omega_0^2 \tag{66}$$

$$H = -\frac{\lambda}{2}(\omega^2 + \omega_0^2) \tag{67}$$

Apply G and H to Equation 60:

$$I(s)_{transient} = \frac{V\omega}{L \cdot Den} \left(\frac{\omega^2 - \omega_0^2}{(s + \frac{\lambda}{2})} - \frac{\frac{\lambda}{2}(\omega^2 + \omega_0^2)}{(s + \frac{\lambda}{2})^2} \right)$$
(68)

Take the inverse Laplace transform of Equation 68:

$$i(t)_{transient} = \frac{V\omega}{L \cdot Den} \left((\omega^2 - \omega_0^2) e^{-\frac{\lambda}{2}t} - \frac{\lambda}{2} t (\omega^2 + \omega_0^2) e^{-\frac{\lambda}{2}t} \right)$$
 (69)

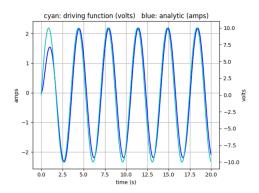


Figure 4: critically-damped transient + steady-state $R=6.0,\,L=1.51,\,C=0.3,\,\omega=1.8,\,V=10$